

**EEM16/CSM51A: Logic Design of Digital Systems**

# Verilog for Combinational Logic

---

Ankur Mehta

[mehtank@ucla.edu](mailto:mehtank@ucla.edu)

Notes attributed to

Yang, Srivastava (UCLA), Mitra & Dally (Stanford)

# Verilog (Hardware Description Language)

---

- Easiest approach
  - Web interface:
    - <https://www.edaplayground.com/>
  - You need to create an account (in order to save your workspace)
- (Optional) Download: The version we are using is from <http://iverilog.icarus.com/> v0.9.7
  - Instructions for downloading and installing for all kinds of platforms:
    - [http://iverilog.wikia.com/wiki/Installation\\_Guide](http://iverilog.wikia.com/wiki/Installation_Guide)
  - For Windows, a nice executable exists:
    - <http://bleyer.org/icarus/>
  - Unfortunately, this packaging does not exist for Macs. I can provide a virtual machine for you to run... albeit a little slower.
- Guides and resources: There are tons of similar guides, e.g.:
  - [http://www.doulos.com/knowhow/verilog\\_designers\\_guide/](http://www.doulos.com/knowhow/verilog_designers_guide/)

# EDA Playground

The screenshot displays the EDA Playground web interface. The top navigation bar includes the EDA Playground logo, buttons for Run, Save, and Copy, and links for Collaborate (beta), Forum, Help, and a user profile for CHIH-KONG KEN Y.

On the left sidebar, the 'Languages & Libraries' section is expanded, showing 'Testbench + Design' with 'SystemVerilog/Verilog' selected, 'UVM / OVM' with 'None' selected, and 'Other Libraries' with 'None', 'OVL 2.8.1', and 'SVUnit 2.11'. The 'Tools & Simulators' section is also expanded, with 'Icarus Verilog 0.9.7' selected and circled in red. Below this, 'Compile & Run Options' shows '-Wall' and 'Run Options' with checkboxes for 'Open EPWave after run' and 'Download files after run'. The 'Examples' section lists 'VHDL' and 'Verilog/SystemVerilog'.

The main editor area contains two code editors. The left editor, titled 'testbench.sv', contains the following code:

```
1 // Testbench
2 module test;
3
4     reg clk;
5     reg reset;
6     reg d;
7     wire q;
8     wire qb;
9
10    // Instantiate design under test
11    dff DFF(.clk(clk), .reset(reset),
12           .d(d), .q(q), .qb(qb));
13
14    initial begin
15        // Dump waves
16        $dumpfile("dump.vcd");
17        $dumpvars(1);
18
19        $display("Reset flop.");
20        clk = 0;
21        reset = 1;
22        d = 1'bx;
23        display;
24
25        $display("Release reset.");
26        d = 1;
27        reset = 0;
28        display;
29
30        $display("Toggle clk.");
```

The right editor, titled 'design.sv', contains the following code:

```
1 // Design
2 // D flip-flop
3 module dff (clk, reset,
4            d, q, qb);
5     input    clk;
6     input    reset;
7     input    d;
8     output   q;
9     output   qb;
10
11     reg      q;
12
13     assign qb = ~q;
14
15     always @(posedge clk or posedge reset)
16     begin
17         if (reset) begin
18             // Asynchronous reset when reset goes high
19             q <= 1'b0;
20         end else begin
21             // Assign D to Q on positive clock edge
22             q <= d;
23         end
24     end
25 endmodule
```

At the bottom of the interface, there are buttons for 'Log' and 'Share', and a status bar showing 'D flip-flop(1)'.

# What is Verilog?

---

- HDL: Hardware description language
  - A way to describe digital (CMOS) hardware.
- Allows abstraction
  - Describe logic in different levels of detail and expression
  - Work at a level to test out ideas
- Enables hierarchy of building blocks (nesting)
  - Complexity and implementation details of a block depends on the stage of the design
  - Can be at any abstraction level
- Execution engine to check the logical behavior of a function.
  - Checks the implementation at each level

**Behavioral**     **case(), always@(), ...**

**Data Flow**     **A+B, A\*B, ...**

**Gate Level**     **AND, OR, NAND ...**

**FET Level**     **NMOS, PMOS**

# HDL $\neq$ high level programming language

---


- The description of the design is physically mapped to actual hardware blocks.
  - Variables and parameters are actual wires and signals or registers that hold state
  - Only representation for variables are bits
- ... with some extensions for convenience when testing / debugging
  - Loops, integers, strings, etc.
  - Only available when verifying a block.
- “Program” not sequential.
  - Modules/Blocks operate in parallel.
    - Signals communicate between modules
  - ... but with support to model delays
  - ... with some extensions for convenience when verifying

C / Python	Verilog
Procedures / function	Modules
Parameters	Ports
Variables	Wires / Regs
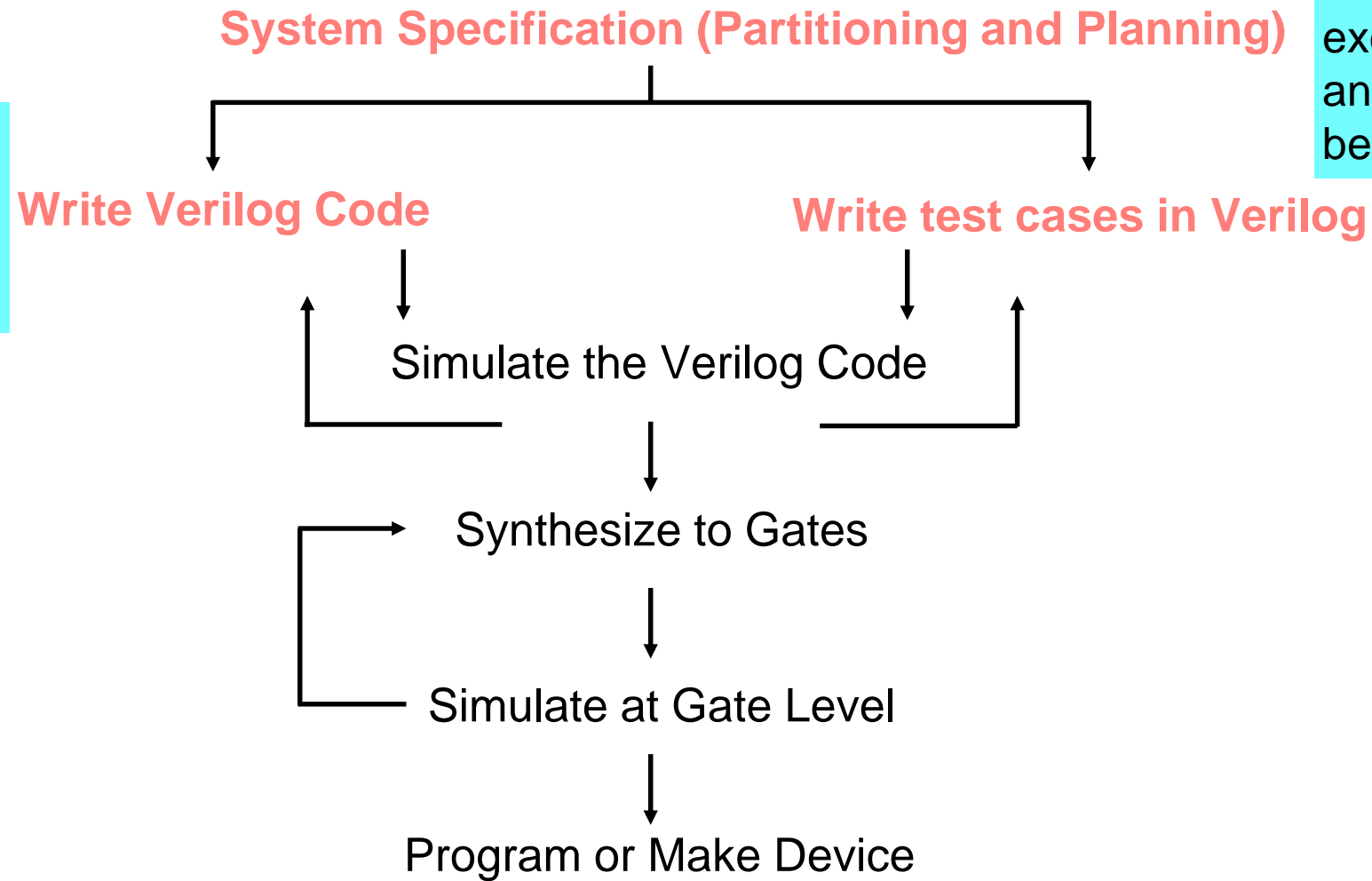
# Design Flow Using Verilog


• **Design:** Code here must be “synthesizable” (can be mapped to hardware)

**TestBench:** Code here exercises the Design and can be entirely behavioral.




# Design Flow Using Verilog

---

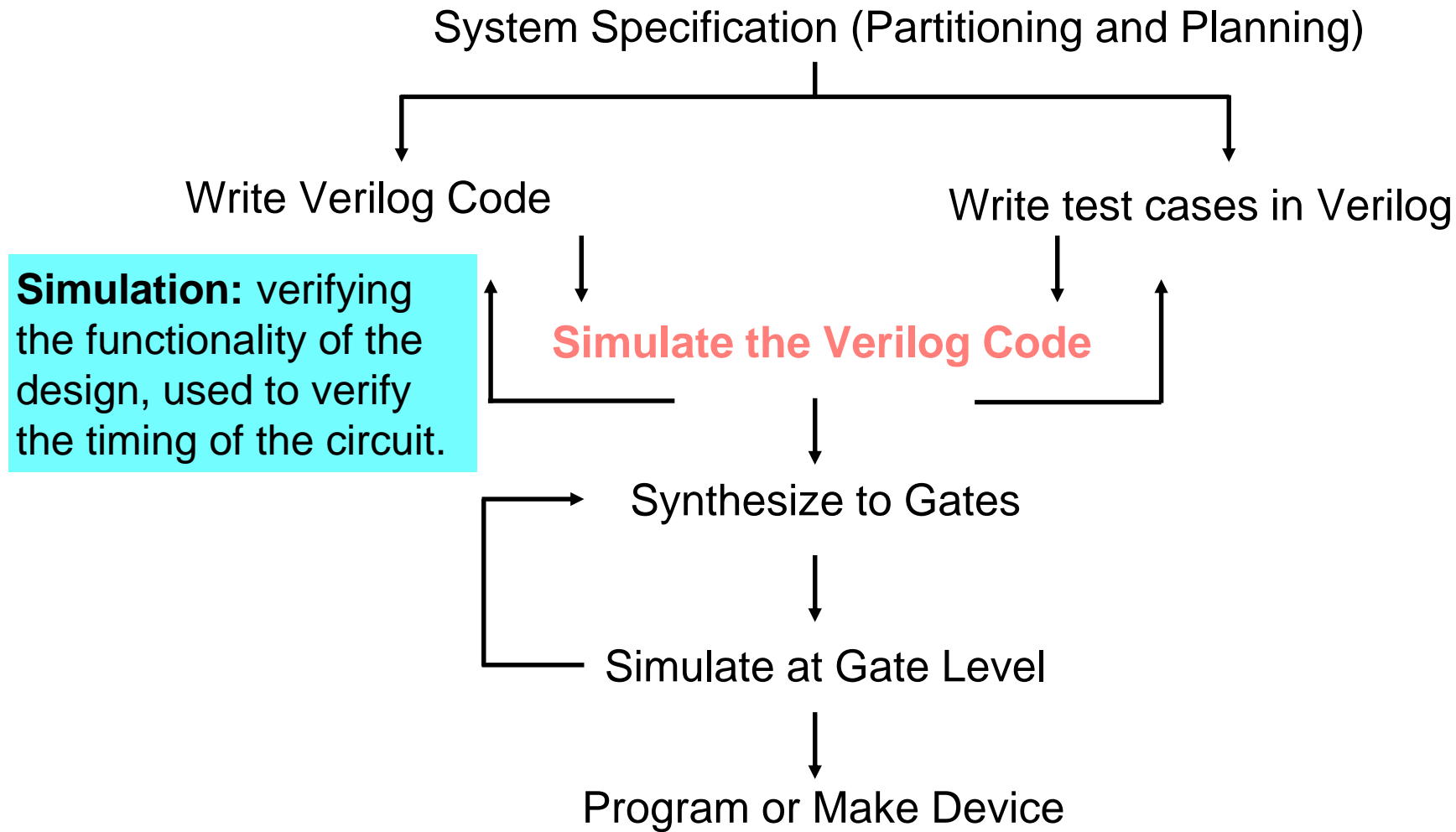


# Design Flow Using Verilog

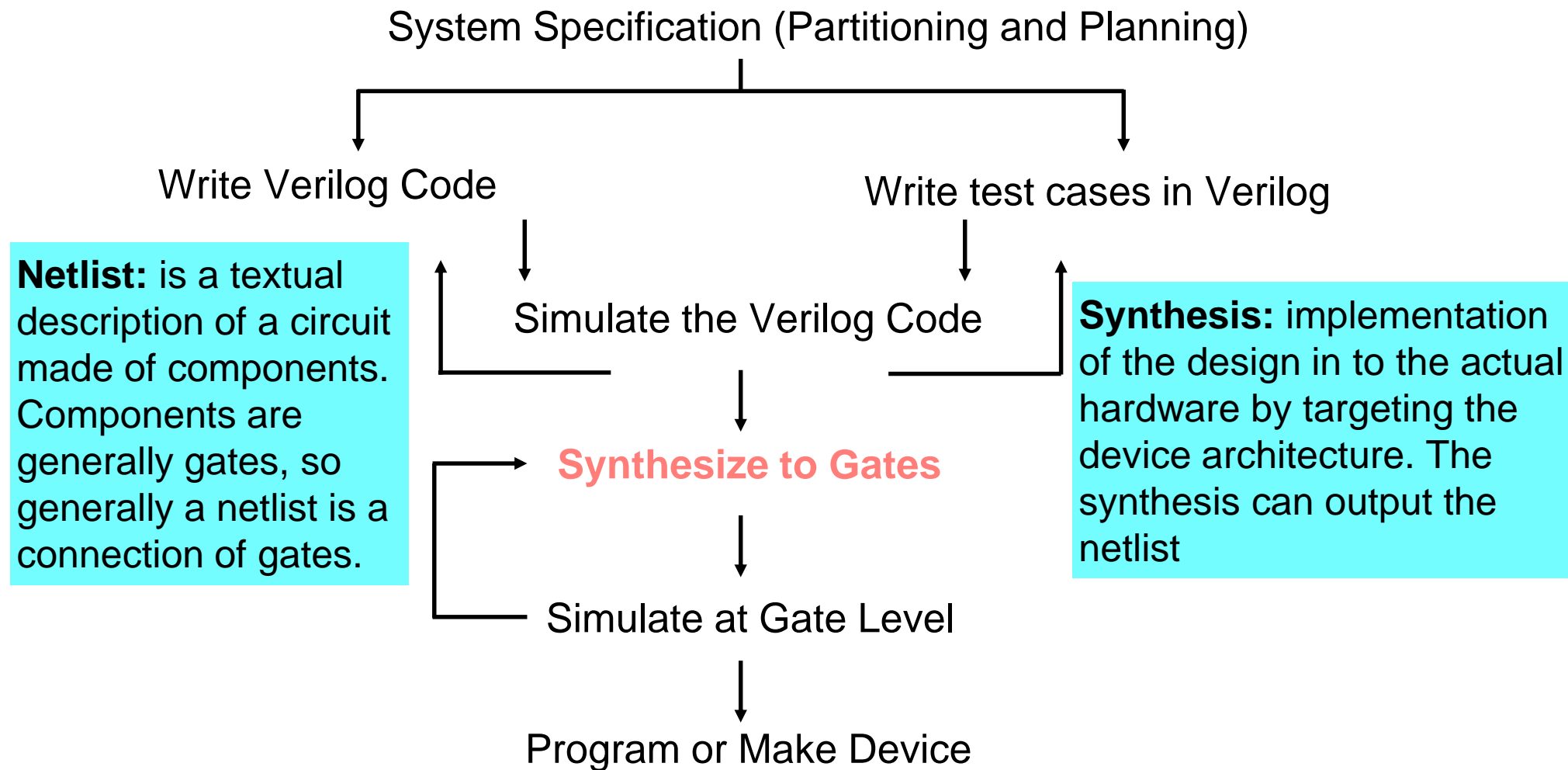



# Design Flow Using

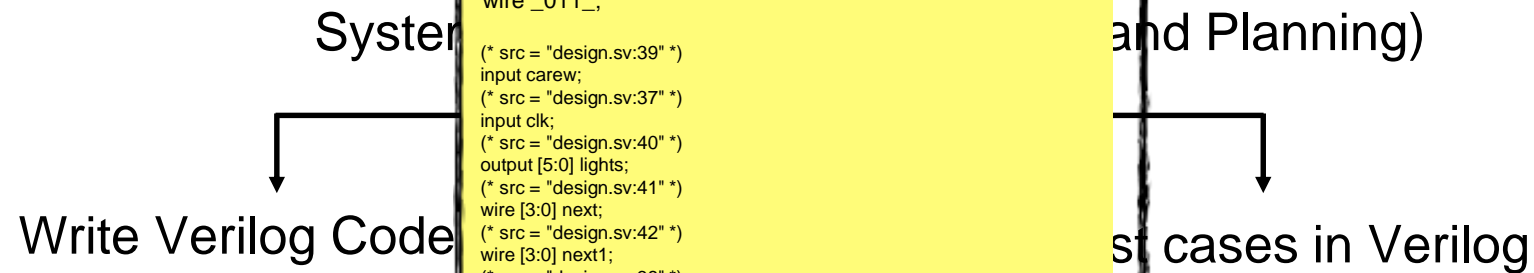

**Netlist:** is a textual description of a circuit made of components. Components are generally gates, so generally a netlist is a connection of gates.

**Synthesis:** implementation of the design in to the actual hardware by targeting the device architecture. The synthesis can output the netlist


```
module traffic_light(clk, rst, carew, lights);
```

```
wire _000_;  
wire _001_;  
wire _002_;  
wire _003_;  
wire _004_;  
wire _005_;  
wire _006_;  
wire _007_;  
wire _008_;  
wire _009_;  
wire _010_;  
wire _011_;
```

```
(* src = "design.sv:39" *)  
input carew;  
(* src = "design.sv:37" *)  
input clk;  
(* src = "design.sv:40" *)  
output [5:0] lights;  
(* src = "design.sv:41" *)  
wire [3:0] next;  
(* src = "design.sv:42" *)  
wire [3:0] next1;  
(* src = "design.sv:38" *)  
input rst;  
(* src = "design.sv:41" *)  
wire [3:0] state;  
NOR _047_ (  
    .A(state[3]),  
    .B(state[2]),  
    .Y(_000_)  
);  
NOT _048_ (  
    .A(state[1]),  
    .Y(_001_)  
);  
NOR _049_ (  
    .A(_001_),  
    .B(state[0]),  
    .Y(_002_)  
);  
NAND _050_ (  
    .A(_002_),  
    .B(_000_),  
    .Y(_003_)  
);  
NOT _051_ (  
    .A(state[0]),  
    .Y(_004_)  
);  
NOR _052_ (  
    .A(state[1]),  
    .B(_004_),  
    .Y(_005_)  
);  
NAND _053_ (  
    .A(_005_),  
    .B(_000_),  
    .Y(_006_)  
);  
NAND _054_ (  
    .A(_006_),  
    .B(_003_),  
    .Y(_007_)  
);
```


# Design Flow Using Verilog

---

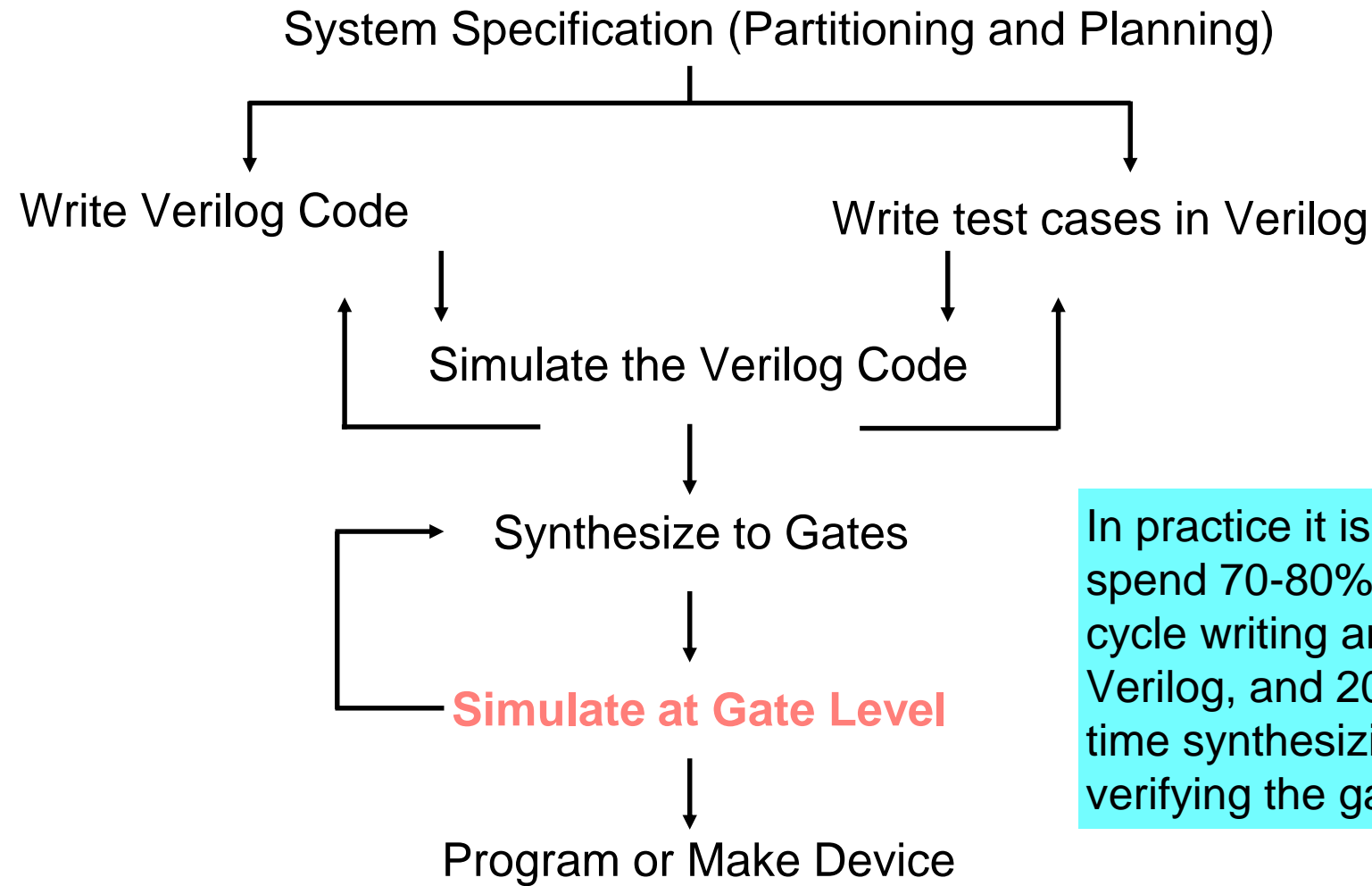


In practice it is common to spend 70-80% of the design cycle writing and simulating Verilog, and 20-30% of the time synthesizing and verifying the gates.

# Design Flow Using Verilog

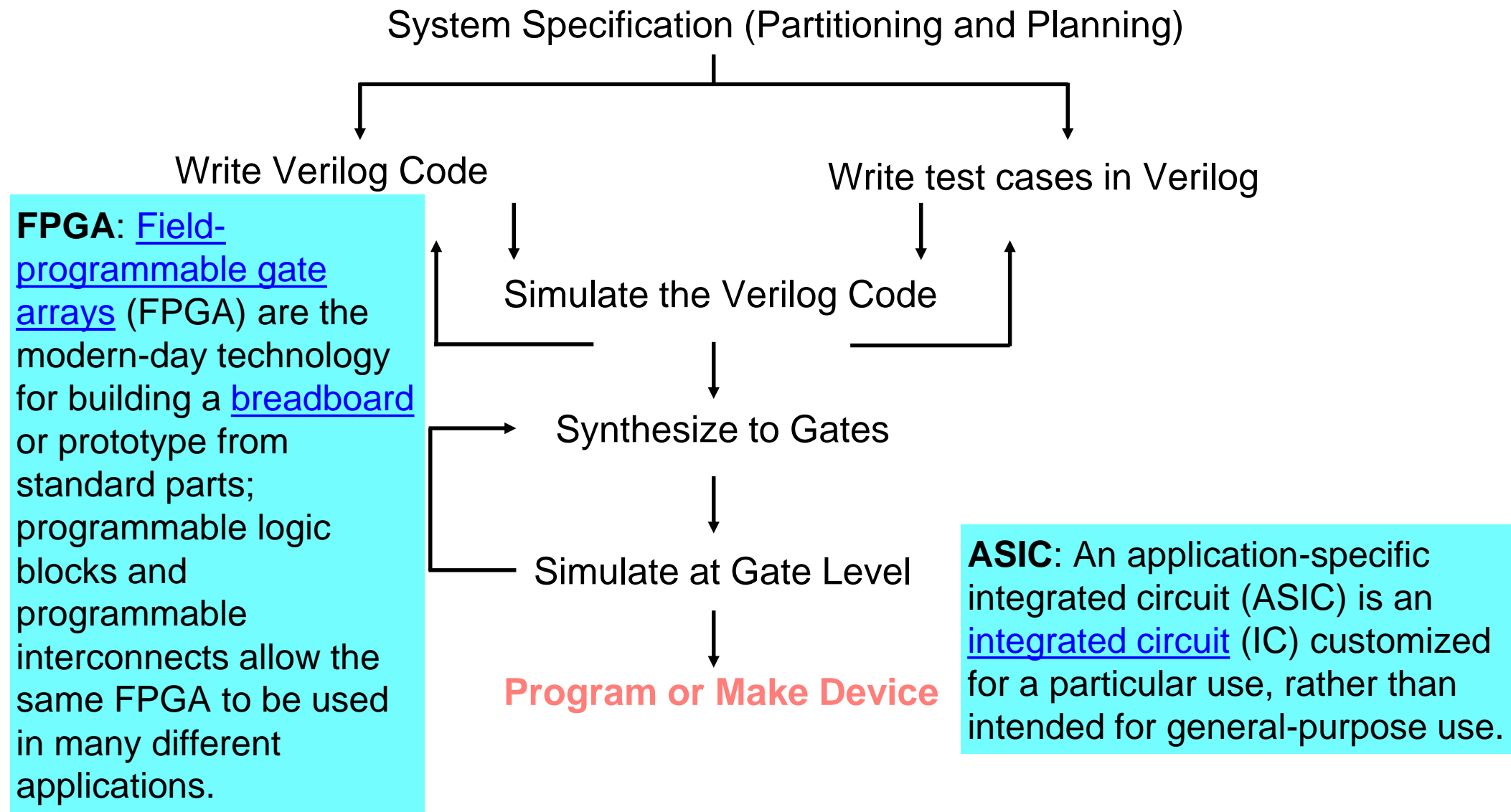

# Design Flow Using Verilog

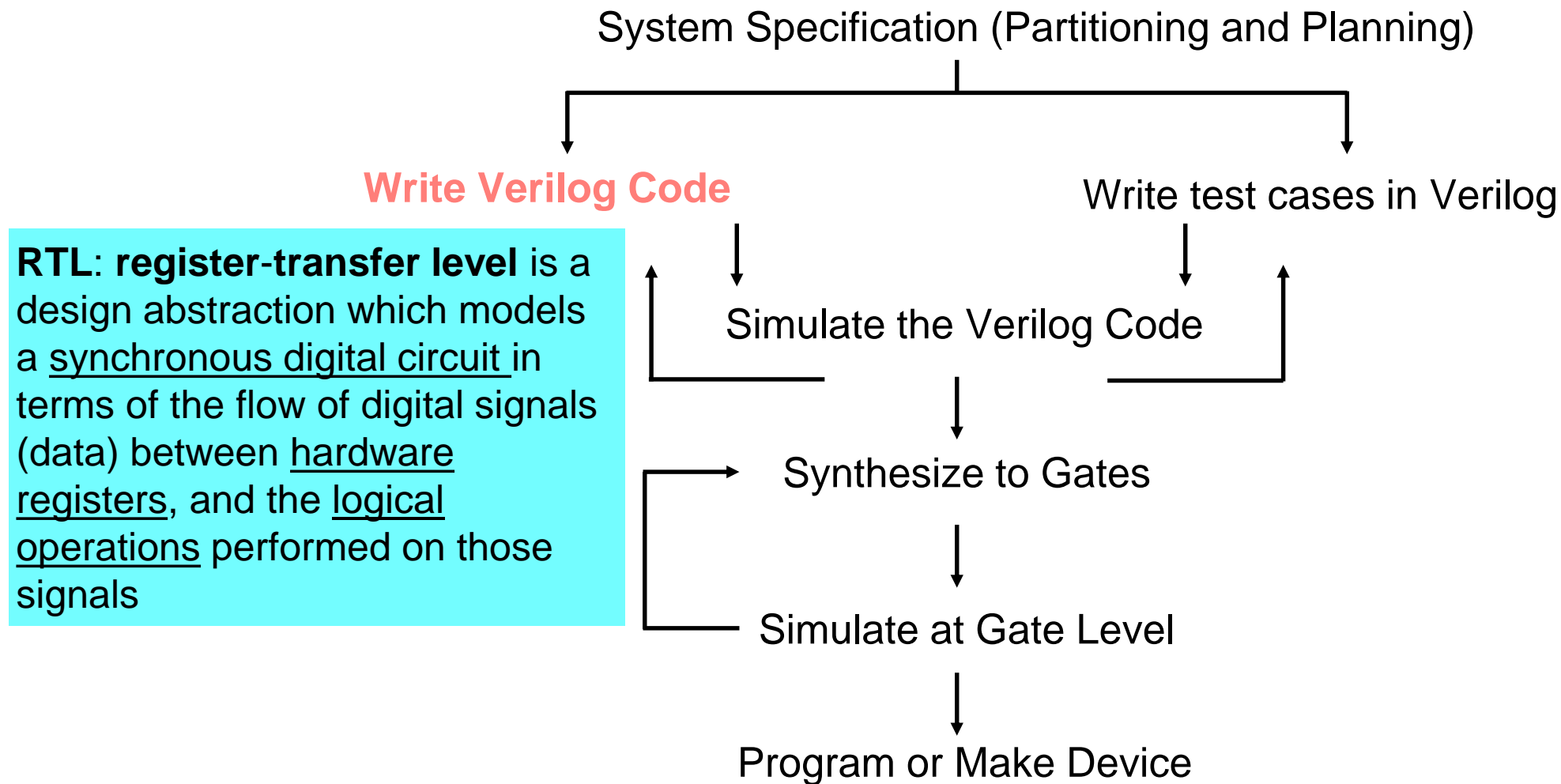

# Modules – Basic Building Block

---

Keyword:  
`module`  
`endmodule`

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);
```

```
endmodule
```

# Modules – Basic Building Block

---

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);
```



Ports

```
input clk, enable ; //in-line comments - use liberally
input [width-1:0] rx_data;
output [width-1:0] tx_data ;
inout [width-1:0] io_data ; //not used much in this class
```



Declare the port variables  
Keywords: **input**, **output**,  
**inout**

```
endmodule
```

# Modules – Basic Building Block

---

Compile time  
parameters  
Keyword:  
**parameter**



```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);  
  
    parameter width = 8; parameter len = 2 ;  
    //parameters are variable replacement during compilation  
  
    input  clk, enable ; //in-line comments - use liberally  
    input  [width-1:0] rx_data;  
    output [width-1:0] tx_data ;  
    inout  [width-1:0] io_data ; //not used much in this class  
  
endmodule
```

# Modules – Basic Building Block

---

Two ways for  
comments  
Single/multi-  
lines

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);
```



```
parameter width = 8; parameter len = 2 ;  
//parameters are variable replacement during compilation
```

```
input clk, enable ; //in-line comments - use liberally  
input [width-1:0] rx_data;  
output [width-1:0] tx_data ;  
inout [width-1:0] io_data ; //not used much in this class
```

```
{  
/*  
Multi-line comment  
begin code here to describe the logic  
end code  
*/  
endmodule
```



# Modules – Basic Building Block

---

Internal signals:  
wires and  
registers

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);

parameter width = 8; parameter len = 2 ;
//parameters are variable replacement during compilation

input clk, enable ; //in-line comments - use liberally
input [width-1:0] rx_data;
output [width-1:0] tx_data ;
inout [width-1:0] io_data ; //not used much in this class

{ // instantiate any internal signals
  wire [width-1:0] int_data; //vector of wires for communicating
  reg [width-1:0] int_reg [0:7]; //an array of vectors - only for reg
  /*
    Multi-line comment
    begin code here to describe the logic
    end code
  */
}
endmodule
```

- Keyword “**wire**”
  - Connecting element between modules.
  - input/outputs are basically wires
  - Can assign logic (no state)
- Keyword “**reg**”
  - Stateful variable (for storage)
  - Can be used for pure combinational logic or sequential logic

# Modules – Basic Building Block

Vectors or  
busses  
[high:low] bit-  
position

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);

parameter width = 8; parameter len = 2 ;
//parameters are variable replacement during compilation

input clk, enable ; //in-line comments - use liberally
input [width-1:0] rx_data;
output [width-1:0] tx_data ;
inout [width-1:0] io_data ; //not used much in this class

// instantiate any internal signals
wire [width-1:0] int_data; //vector of wires for communication
reg [width-1:0] int_reg [0:7]; //an array of registers - only for sequential logic
/*
Multi-line comment
begin code here to describe the logic
end code
*/
endmodule
```

Array of 8 registers  
[low:high]  
Only for reg

- Keyword “**wire**”
  - Connecting element between modules.
  - input/outputs are basically wires
  - Can assign logic (no state)
- Keyword “**reg**”
  - Stateful variable (for storage)
  - Can be used for pure combinational logic or sequential logic

# Modules – Basic Building Block

---

```
module BuildingBlock (clk, enable, rx_data, tx_data, io_data);

parameter width = 8; parameter len = 2 ;
//parameters are variable replacement during compilation

input clk, enable ; //in-line comments - use liberally
input [width-1:0] rx_data;
output [width-1:0] tx_data ;
inout [width-1:0] io_data ; //not used much in this class

// instantiate any internal signals
wire [width-1:0] int_data; //vector of wires for communicating
reg [width-1:0] int_reg [0:7]; //an array of vectors - only for reg
/*
    Multi-line comment
    begin code here to describe the logic
    end code
*/
endmodule

module test;
//Instantiate
reg [7:0] rx1, BB8_data, tx, io;
reg en; //either stateful register or logic signal

//longer form and ordering doesn't matter
BuildingBlock BB8(.clk(gclk), .enable(en),
                  .rx_data(rx1), .tx_data(BB8_data),
                  .io_data(io));

//shorter but ordering matters
BuildingBlock BB10( gclk, en, BB8_data, tx, io),
endmodule
```

Two ways to instantiate

- 1) passes in overriding parameters (in order)
- 2) port ordering matters

# Signals, Numbers and Variables

---

- Numbers are represented as `<length>'<base><value>`
  - Examples: `8'b00010111`, `2'hFF`, `4'd1234`, `8'b0001_0111` (“\_” improves readability)
  - High impedance “z” (“?” is accepted in Verilog)
    - not driven by an output
    - default starting value of nodes
  - Undefined – “x”
    - not sure which value it is (usually because 2 nodes are driving it and conflicting)
    - Good to identify this for debugging
- Port/Variable naming
  - Try to choose meaningful names.
  - Lots of different naming standards.
    - Example: `<name>_i` are inputs, `<name>_o` are outputs, `<name>_w` are wires, etc.
  - Account for assertion (`unHappy_L` for assert low... 0=true)

# Ways to Describe A Function/Block

---

- Structural
  - Consists only of module calls
- Declarative
  - Concurrently executed combinational logic
- Procedural
  - Sequentially executed program
    - A state machine (with storage) ... More later...
    - Or combinational logic
- ~~Functional/Task~~
  - ~~Function calls~~
  - ~~Not mapped to hardware so we ignore this~~

# Structural Description

---

```
module system;
  wire [7:0] bus_v1, const_s1;
  wire [2:0] regSpec_s1, regSpecA_s1,
    regSpecB_s1;
  wire [1:0] opcode_s1;
  wire Phi1, Phi2, writeReg_s1,
    ReadReg_s1, nextVector_s1;
  clkgen clkgen1(Phi1, Phi2);
  datapath datapath1(Phi1, Phi2,
    regSpec_s1, bus_v1, writeReg_s1,
    readReg_s1);
  controller controller1(Phi1, Phi2,
    regSpec_s1, bus_v1, const_s1,
    writeReg_s1, readReg_s1,
    opcode_s1, regSpecA_s1,
    regSpecB_s1, nextVector_s1);
  patternsource patternsource1(Phi1,
    Phi2, nextVector_s1, opcode_s1,
    regSpecA_s1, regSpecB_s1,
    const_s1);
endmodule
```


- Lowest level of abstraction
- Compose a module out of module calls.
  - Specify components, and wiring
- Maps a physical structure into Verilog.
  - One example to the right
- Hierarchical
  - List of modules/blocks
  - List of sub-blocks.
  - List of gates
  - List of transistors.
- Typically don't go below a gate level list.
  - Only near the end of a design.
  - We'll use it to implement functions as logic gates for the purposes of this class.

# Declarative Statements

- Provides the logical relations between inputs and outputs.
- Assign outputs to be some function of the inputs (*continuously*)
  - Denoted by the key word is ***assign***
- Uses a C-like expression syntax
- Examples (*all execute in parallel*):

```
wire      nor, a, o, out;  
wire [4:0] sum;  
...  
assign    nor = ~(b | c);  
assign    a = x & y, o = x | y;  
assign    sum[4:0] = a[3:0] + b[3:0];  
assign    out = (sel) ? in1: in2; //conditional
```

 assign models wires to  
be outputs of  
combinational logical  
elements



- Outputs are wires, and can be a single bit or multiple bits.
  - It is good practice to declare all variables even though Verilog allows undeclared single bit wires.

# Declarative Order of Execution


---

- All assigns can be presumed to happen simultaneously
  - Each statement is occurring concurrently.  
assign x = a;  
assign a = b;
  - In C, the order of the above statements matters, but not in Verilog.
    - Above example, x = b no matter what because both statements are wires shorting those signals.
  - Consider the wiring  
assign out = a;  
assign out = b;
    - This yields a warning and is not allowed.


 
# Example

- In In this module body, there are four continuous assignment statements.
- And-Or-Invert gate.
  - Note the alternate module declaration
- module AOI (  
    input A, B, C, D,  
    output     F  
);
- The assign statements are independent and executed concurrently.
  - **Non-Blocking assignment**
  - Any change of any of the inputs causes a re-evaluation of the statement.



```
// Verilog code for AND-OR-INVERT gate
module AOI (input A, B, C, D, output F);
    wire F; // the default
    wire AB, CD, O; // necessary

    assign AB = A & B;
    assign CD = C & D;
    assign O = AB | CD;
    assign F = ~O;
endmodule
// end of Verilog code
```

# Shifting and Concatenation

- Shifting:

- Let  $x[7:0] = 8'b0101\_1101$   
(Right shift by 1)  $X>>1$   
(Left shift by 2)  $X<<2$

0010\_1110  
0111\_0100

Fills with 0's and not wrap around

- Concatenation

- Format: {operand, ... , operand} or {(#){operand}}
- Let  $A=3'b111$ ,  $B=3'b010$ ,  $C=3'b011$ ,  $D=3'b100$ ,  $E=8'b1010\_1010$

{B,C}                    6'b010001  
{A,B,3'b001}        9'b111010001  
{A,B[0],C[1]}       5'b11101  
{(3){D[2]}}         3'b111

{(3){E[7]},E[7:2]} 8'b1111\_0101

Copies operand # times

A shift ( $>>4$ ) that extends the MSB.  
Sign extension!  
A straight  $>>$  would not be correct.

- Outputs must be sized to the right vector length

# Operators

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	multiply
	/	divide
	+	add
	-	subtract
	%	modulus
	+ -	unary plus unary minus
Logical	!	logical negation
	&&	logical and
		logical or
Equality	==	equality
	!=	inequality
	===	equality w/ {x,z}
	!==	inequality w/ {x,z}

Not synthesizable

Operator Type	Operator Symbol	Operation Performed
Bit-wise	~	bitwise negation
	& ( )	bitwise and (or)
	^ (^~ or ~^)	bitwise ex-or (ex-nor)
Reduction	& ( ) ~& (~ ) ^ ^~ or ~^	reduction and (or) reduction nand (nor) reduction ex-or reduction ex-nor
Relational	> (<)	greater (less) than
	>=	greater than or equal
	<=	less than or equal
Concatenation	{ }	concatenation
Conditional	<cond>?<>:<else>	conditional
Shift	>>	right shift
	<<	left shift
	>>>	arithmetic right shift
	<<<	arithmetic left shift

Operates on all bits of a vector

w/ sign extension may be non-synthesizable

# Procedural Statements

---

- Flow control (implies sequential ordering)
  - Denoted with keyword ***always*** or ***initial*** provides functionality of a tiny program that executes sequentially.
- “initial”
  - Purely behavioral for test bench
  - The sequence that is run only at the **beginning** of execution.
- “always”
  - Can sometimes be synthesized.
  - Each always block is run concurrently and executed whenever it is activated.
  - always @( <activation list>)

# Procedural Statements

---

- Inside an *initial* or *always* block, can use standard control flow statements:

```
if (<conditional>) then
    <statements>; //statements can be compound by using begin <statements>; end
else
    <statements>;
```

```
case (<var>)
    <value1>: <statements>;
    <value2>: <statements>;
    ...
    default: <statements>
```

# Procedural Statements

---

- Ones that are purely for behavioral modeling and not synthesizable

```
for (i = 0; i < 256; i = i + 1) begin  
    <statements>;  
end
```

```
while (<conditional>) begin  
end
```

```
repeat (<number>) begin  
end
```

# Always example

---

- Example:

```
reg out;  
always @ (reset)
```

Output must be  
a reg

```
begin
```

```
// more than 1 statement allowed inside here
```

```
if (x==y) then
```

```
    out = in1;
```

```
else
```

```
    out = in2;
```

```
end
```

Inputs can be  
either wires or  
reg

# Always Block For Combinational Logic

---

Let's make an "always" block implement a combinational logic

- No unset outputs

- Are all outputs given a value with an explicit assignment statement at the end of the block?
  - If not, then it is unset.
- If the output is ***always set***, then the always block **forms combinational logic**.
- If you leave it unset, it implies the previous value => storage

- Make it activate for all input transitions.

- ***Activation list determines when to execute the block***
- So, make a complete list of all conditional and RHS variables (inputs) in the activation list

```
always @ (x or y or in1 or in2)
```

```
begin
```

```
    // more than 1 statement allowed inside here
```

```
    if (x==y) then
```

```
        out= in1;
```

```
    else
```

```
        out = in2;
```

```
end
```



# More About Activation Lists

---

- Tells the simulator when to run this block
  - Allows the user to specify when to run the block and makes the simulator more efficient.
  - But also enables subtle errors to enter into the design.
- Two forms of activation list in Verilog:
  - @(signalName1 or signalName2 or ...)
    - Evaluate this block when any of the named signals change (either positive or negative change)
  - @(posedge signalName1) or @(negedge signalName2)
    - Makes something trigger on the transition of a signal (register).
    - Evaluates only on one edge of a signal.
    - Can have @(posedge signal1 or posedge signal2)
      - Edges are singular events so must be “or”
      - Don't use because difficult to map to an actual gate
- You can use always @(\*)
  - All inputs considered (short-cut)
  - Use comma's instead of or's @(signalName1, signalName2, ...)
- You cannot use always without an activation list.
  - Leads to an infinite loop

# More Examples

- *if* statement
- What happens if no *else*?
  - `reg f;` //means that *f* can keep state.
  - *f* stays the value of a even when *sel* changes to 0.
- Case statement
  - Helps with multiple input multiplexer.
  - Selecting Finite State Machine state transitions.
- *default* covers the condition when not all cases are covered on the LHS.
  - Otherwise, keeps previous value... not combinational logic any more.
  - Example uses it to flag when not all cases are covered.

```
reg f;
always @(sel or a or b)
begin
    if (sel == 1)
        f = a;
    else
        f = b;
end
```

```
module mux (a,b,c,d,sel,y);
input a, b, c, d;
input [1:0] sel;
output y;

reg y;

always @ (a or b or c or d or sel)
case (sel)
    0 : y = a;
    1 : y = b;
    2 : y = c;
    3 : y = d;
    default : $display("Error in SEL");
endcase

endmodule
```

# Different *Cases*

- Normal *case* statements can handle *x*'s and *z*'s
  - Good for debugging to flag these situations
  - Statement3 can be a \$display of error message
- May need to spell out don't care
  - Use "?" or "z"
  - *casez* instead of *case*
  - casez also allows us to keep going despite z's (not realistic)
- May want to keep going despite x's
  - *casex* instead of *case*
  - Treat x's as also don't cares (stat2 selected if mask=11001100)
  - Not as safe for logic synthesis since x's may indicate errors...

```
case (select[1:2])
    2'b00: result = 0;
    2'b01: result = flaga;
    2'b0x,
    2'b0z: result = flaga ? 'bx : 0;
    2'b10: result = flagb;
    2'bx0,
    2'bz0: result = flagb ? 'bx : 0;
    default: result = 'bx;
endcase
```

```
reg [7:0] r, mask;

    •
    •
    •

mask = 8'bx0x0x0x0;
casex (r ^ mask)
    8'b001100xx: stat1;
    8'b1100xx00: stat2;
    8'b00xx0011: stat3;
    8'bx001100: stat4;
endcase
```

```
reg [7:0] ir;

    •
    •
    •


casez (ir)
    8'b1??????? : instruction1(ir);
    8'b01??????? : instruction2(ir);
    8'b00010???? : instruction3(ir);
    8'b000001??? : instruction4(ir);
endcase
```

# Care with *Cases*

- Case statements are actually prioritized
  - The 2<sup>nd</sup> case entry doesn't happen unless after the 1<sup>st</sup> not match.
  - May not be what the actual hardware implies – especially when cases are mutually exclusive.
- Full case
  - All binary possibilities of the selection is covered in the case statements. Otherwise, include a default.
  - Desirable for most combinational logic implementation.
  - Avoid storage of old value (*unless you intentionally want to build a storage element*)
- Parallel case
  - Only one case is triggered for any change in the selection.
  - Again, desirable for most combinational logic implementation.
  - Exception is priority encoder. *You intentionally want to select the first case that hits.*


```
module intctl1a
  (output reg      int2, int1, int0,
   input   [2:0] irq
  );

   always @* begin
    {int2, int1, int0} = 3'b0;
    casez (irq)
      3'b1??: int2 = 1'b1;
      3'b?1?: int1 = 1'b1;
      3'b???1: int0 = 1'b1;
    endcase
  end
endmodule
```



# Building Test Benches

---

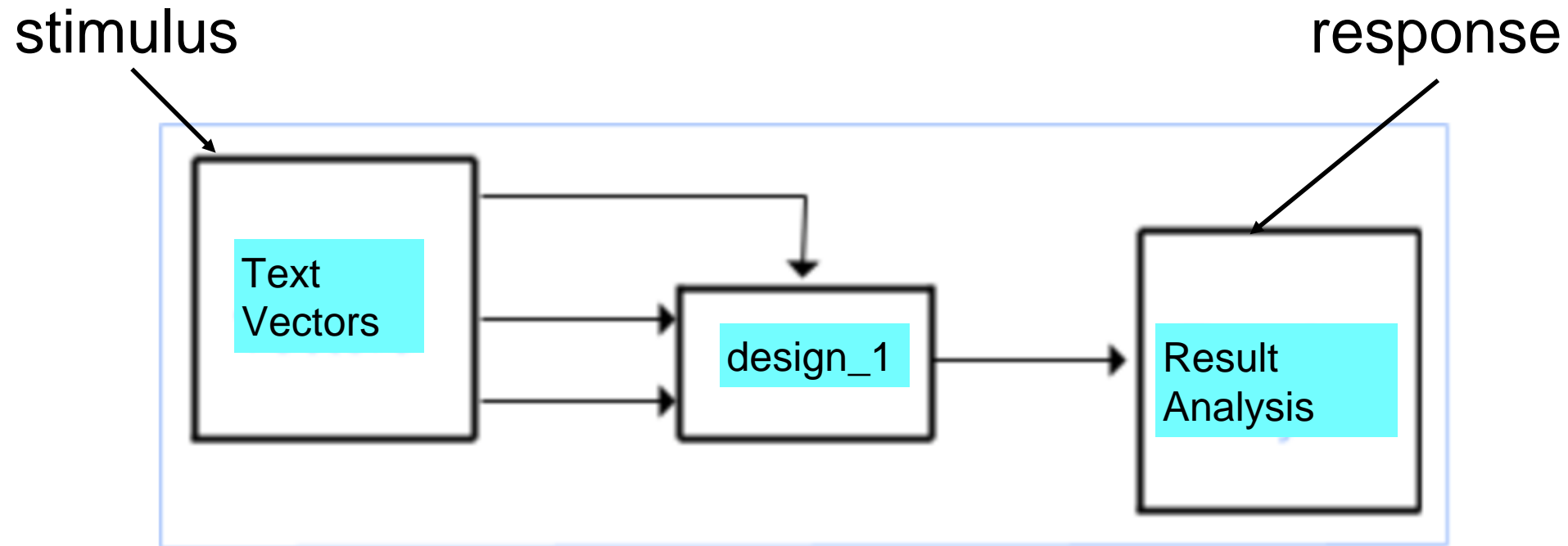

- Test benches help you to verify that a design is correct.
- You can use things in test bench that are not synthesizable because the code of the test bench is not designed to be downloaded on hardware

# Test Benches



---

```
module design_1_test    // No ports!  
  
    initial  
        // Stimulus  
        ...  
  
    design_1 M (SEL, A, B, F);  
  
    initial  
        // Analysis  
        ...  
  
endmodule
```

- Recall the “initial” statement
  - They are not synthesizable
- The stimulus and the response can be coded using a pair of initial blocks or combined in a single initial block.
  - An initial block (like always blocks) contains sequential statements that describe the behavior of signals in a test bench.
  - It's ok to use non-synthesizable looping structures
- In the stimulus, we need to generate waveform on the A, B and SEL inputs
 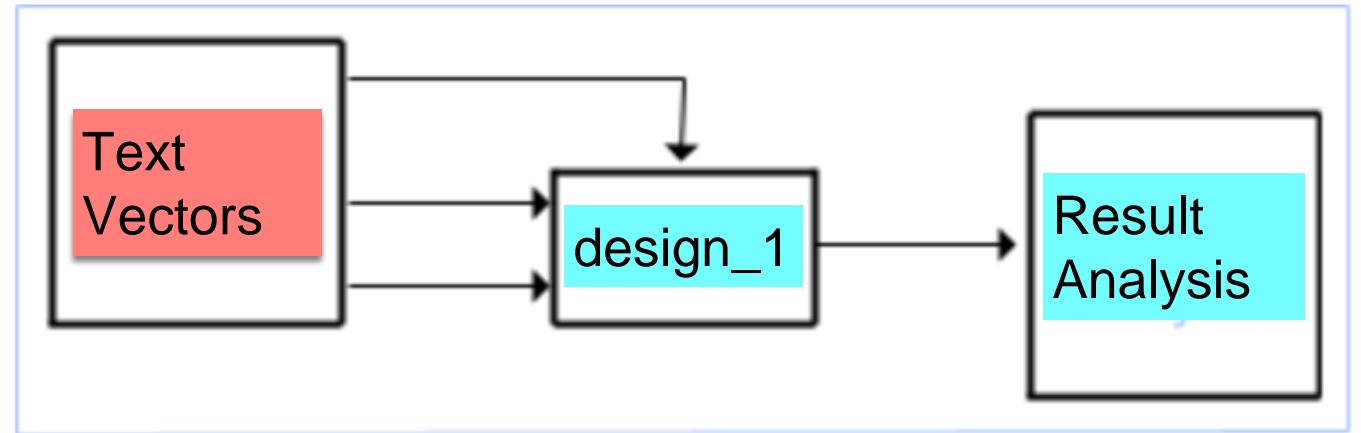
# Test Benches – Stimulus

```
initial // Stimulus
begin
    SEL = 0; A = 0; B = 0;
    #10 A = 1;
    #10 SEL = 1;
    #10 B = 1;
end
```



- SEL = 0; A = 0; B = 0;
  - Contains three sequential statements. SEL is set to 0, then A, then B. All three are set to 0 at time = 0.
- #10 A = 1; #10 SEL = 1; #10 B = 1;
  - The notation is to force the simulator to advance in time for a Test Bench to execute a sequence of events.
  - 10 time units after A is set to 1, SEL is set to 1.
  - Another 10 time units later (so we are now at simulation time = 30 time units), B is set to 1.

# A Note on Delays in Verilog

---


- Verilog simulated time is in “units” or “ticks”.
- `timescale 1ns/10ps defines the ticks to be 1ns (the internal time step is 1/100<sup>th</sup>)
- Simulated time
  - Unrelated to the wall-clock to run the simulator.
  - Models the time in the modeled machine
    - When the computer completes with all the “events” that occur at the current simulated time
    - The computer increases time until another signal is scheduled to change values.
- User must specify delay values explicitly to Verilog
  - # delayAmount (not synthesizable)
    - When the simulator sees this symbol, it stops “evaluating” the particular expression and schedules the delayAmount of simulated time (# of ticks) to enact the change in the signal.
    - Delays are used to model the delay in functional units (in synthesized designs)
  - Can be tricky to use properly
- The standard cell library contains annotate delay information.
  - Synthesized results can have realistic delay simulation


 
# Delay Control


---

- Can be tricky so don't use it except in Test Bench
- Declarative – “*Delayed Assignment*”
  - Make out a delayed version of the input (by 10 ticks) in an assign or wire statement.  
assign #100 out = in;
  - Anywhere else to put delay is not allowed
- Procedural – “*Delayed Evaluate*”
  - always @(phi or in)  
#100 if (phi) then out = in;
  - Wait 100 ticks after either input changes, then checks to see if phi == 1, and then updates the output.
  - Example – clock source  
always  
#100 out = ~out;
  - An always block is not reactivated until every line of code is evaluated (or cause an event to be scheduled).
    - So while waiting for the delayed event, new inputs are ignored.


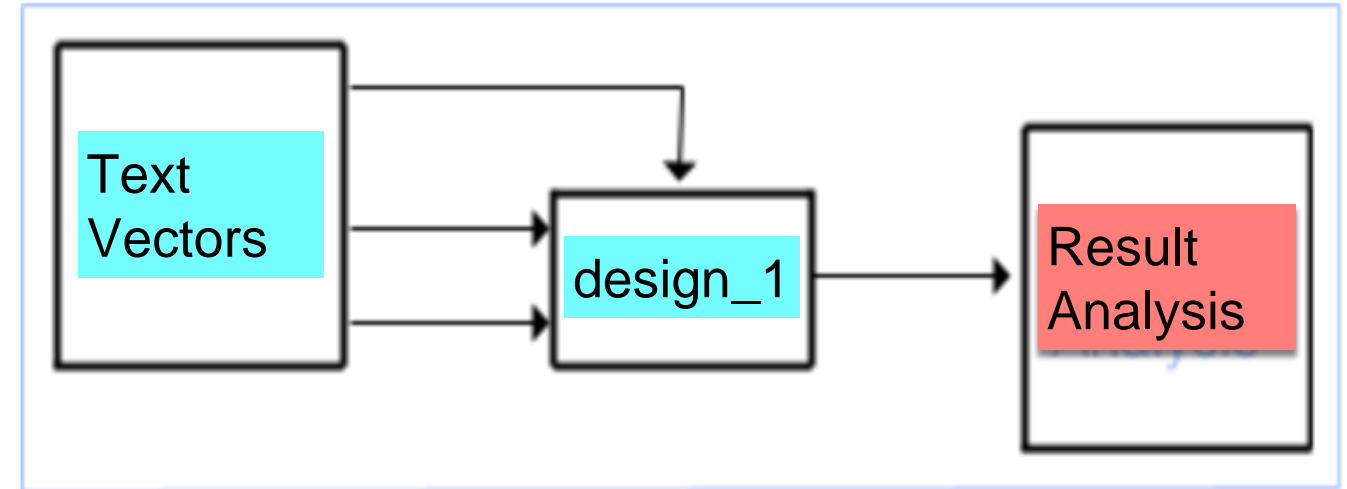
# Test Benches – Responses

```
initial // Response
    $monitor($time, , SEL, A, B, F);
```



- `$monitor` is a system task that is part of the Verilog language.
  - Print values to the screen corresponding to the arguments that you pass to the task when it is executed.
  - The `$monitor` task is executed whenever any one of its arguments changes.
- `$time` is a system function. It returns the current simulation time.
  - In the above example, `$time` is an argument to `$monitor`.
  - However, `$time` changing does not cause `$monitor` to execute - `$monitor` does not print to the screen the values of all of the arguments every time the simulation time changed.
- `$display("test\n")` is a function that prints the words "test" when executes.
- Waveform viewers are also available which can be easier.

```
0 0000
10 0101
20 1100
30 1111
```

# Example of Test Bench

```
`timescale 1ns/10ps // specify system timescale
`define TCK 2 // define 2ns clock period
module TestClkAdder ; // name of testbench
reg [3:0] A_i, B_i ; reg CLK ; wire [3:0] S_o ; integer i ; // declare variable
CLKADD U00(.SUM(S_o), .AI(A_i), .BI(B_i),.CLK(CLK)) ; // instantiate design
reg [7:0] TestVec [0:511] ; // declare an array to store 512 8-bit test data
initial CLK = 0 ; always #(0.5*`TCK) CLK = ~CLK ; // generate clock
initial begin // start simulation
$readmemb("TestData.txt", TestVec) ; // read data from external .txt file
$display("*** Clocked-Adder Simulation Starts *** \n") ;
$monitor("Time=%g, S=%d, A=%d, B=%d", $time, S_o, A_i, B_i);
for(i=0; i<512; i=i+1) // feed data into design for 512 cycles
    #(`TCK+0.2) {A_i,B_i} = TestVec[i] ;
    #(`TCK) $finish ; // finish the simulation
end
endmodule
```

`timescale – defines a “tick” to 1ns

`define – for global variables

Produces 010101... indefinitely



Reads a text file  
into an array

# Example From Lecture – 4-bit Prime-or-1

---

		a			
		00	01	11	10
c	dc	0 <sub>0</sub>	1 <sub>1</sub>	1 <sub>3</sub>	1 <sub>2</sub>
	00	0 <sub>4</sub>	1 <sub>5</sub>	1 <sub>7</sub>	0 <sub>6</sub>
	01	0 <sub>12</sub>	1 <sub>13</sub>	0 <sub>15</sub>	0 <sub>14</sub>
	10	0 <sub>8</sub>	0 <sub>9</sub>	1 <sub>11</sub>	0 <sub>10</sub>
		b			

# Example from Lecture – 4-bit Prime

  

# Example From Lecture – 4-bit Prime

---

Using case

```
module prime(in, isprime) ;  
    input [3:0] in ; // 4-bit input  
    output isprime ; // true if input is prime  
    reg isprime ;  
  
    always @(in) begin  
        case(in)  
            1,2,3,5,7,11,13: isprime = 1'b1 ;  
            default: isprime = 1'b0 ;  
        endcase  
    end  
endmodule
```

Here you described  
what you want, not  
how to design it

# Example From Lecture – 4-bit Prime

---

Using **case**x

```
module prime1(in, isprime) ;
    input [3:0] in ;           // 4-bit input
    output      isprime ; // true if input is prime
    reg         isprime ;

    always @(in) begin
        case(x(in))
            4'b0xx1: isprime = 1 ;
            4'b001x: isprime = 1 ;
            4'bx011: isprime = 1 ;
            4'bx101: isprime = 1 ;
            default: isprime = 0 ;
        endcase
    end
endmodule
```

# Example From Lecture – 4-bit Prime

---

Using **assign**

```
module prime(in, isprime) ;  
    input [3:0] in ;           // 4-bit input  
    output      isprime ; // true if input is prime  
  
    wire isprime = (in[0] & ~in[3]) |  
                   (in[1] & ~in[2] & ~in[3]) |  
                   (in[0] & ~in[1] & in[2]) |  
                   (in[0] & in[1] & ~in[2]) ;  
  
endmodule
```



# Example From Lecture – 4-bit Prime

---

## Test Bench

```
module test_prime ;  
    reg [3:0] in ;  
    wire isprime ;  
  
    // instantiate module to test  
    prime p0(in, isprime) ;  
  
    initial begin  
        in = 0 ;  
        repeat (16) begin  
            #100  
            $display("in = %2d isprime = %1b",in,isprime) ;  
            in = in+1 ;  
        end  
    end  
endmodule
```

# Example From Lecture – 4-bit Prime

---

## Testing Results

```
# in = 0 isprime = 0
# in = 1 isprime = 1
# in = 2 isprime = 1
# in = 3 isprime = 1
# in = 4 isprime = 0
# in = 5 isprime = 1
# in = 6 isprime = 0
# in = 7 isprime = 1
# in = 8 isprime = 0
# in = 9 isprime = 0
# in = 10 isprime = 0
# in = 11 isprime = 1
# in = 12 isprime = 0
# in = 13 isprime = 1
# in = 14 isprime = 0
# in = 15 isprime = 0
```

# Summary

---

## *References*

- Doulos Verilog:
  - [https://www.doulos.com/knowhow/verilog\\_designers\\_guide/](https://www.doulos.com/knowhow/verilog_designers_guide/)
- EDAPlayground:
  - <http://www.edaplayground.com>